
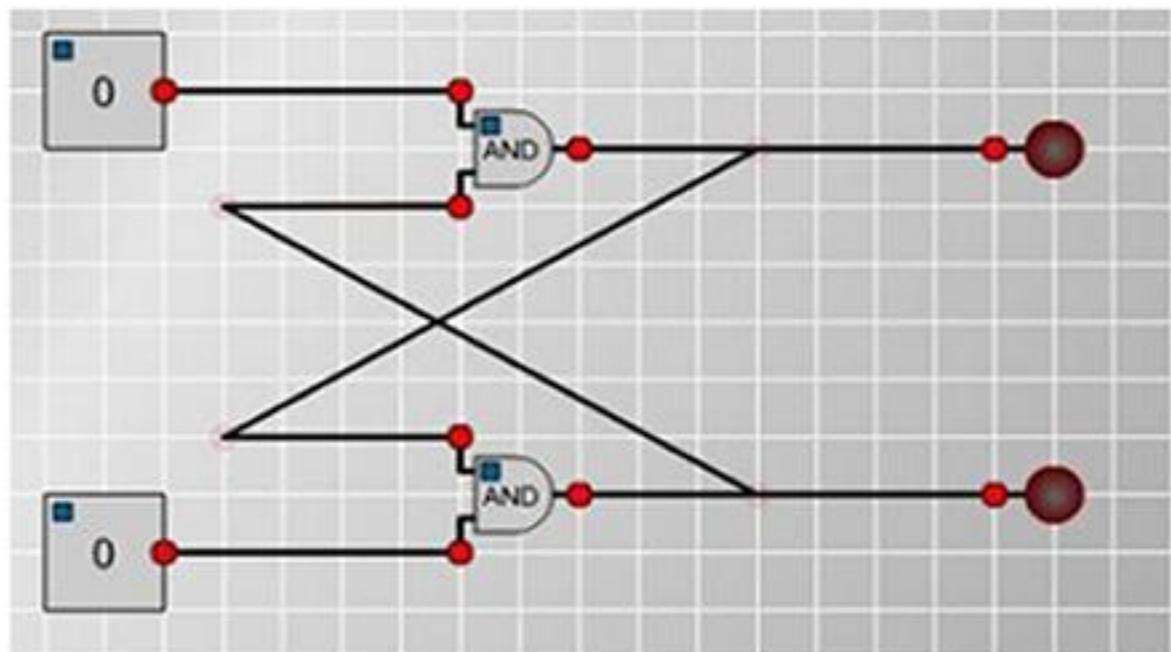


# Circular Circuitry

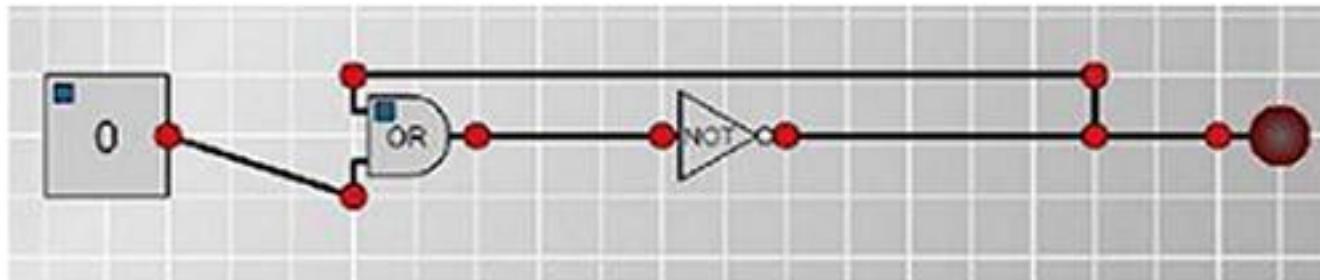

**What will happen  
when you switch on  
these circuits?**

**What will happen if  
the change the gates  
to different types?**



Thousands more problems can be found on  
the NRICH Maths website:  
<http://nrich.maths.org>