
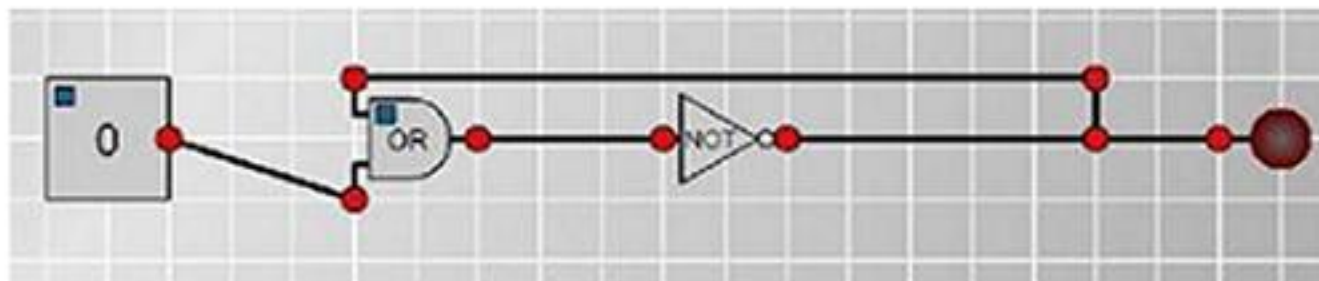


Circular Circuitry

What will happen when you switch on these circuits?

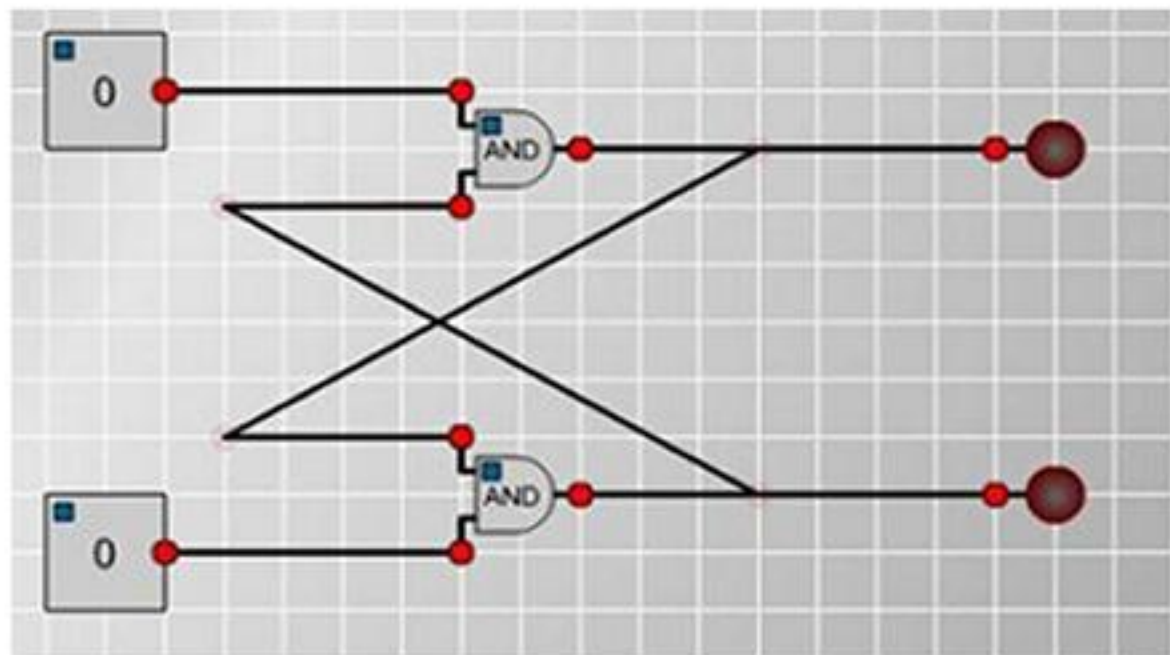What will happen if the change the gates to different types?



Thousands more problems can be found on the NRICH Maths website:

<http://nrich.maths.org>