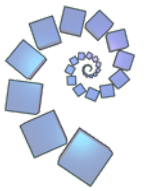


Circular Circuitry



What will happen when you switch on these circuits?

What will happen if you change the gates to different types?

